



UNIVERSITEIT•STELLENBOSCH•UNIVERSITY  
jou kennisvennoot • your knowledge partner

# **E344 Assignment 4**

Michiel Christiaan van der Berg  
22546448

Report submitted in partial fulfilment of the requirements of the module  
Design (E) 344 for the degree Baccalaureus in Engineering in the Department of Electrical  
and Electronic Engineering at Stellenbosch University.

September 6, 2021



UNIVERSITEIT • STELLENBOSCH • UNIVERSITY  
jou kennisvennoot • your knowledge partner

## Plagiaatverklaring / *Plagiarism Declaration*

1. Plagiaat is die oorneem en gebruik van die idees, materiaal en ander intellektuele eiendom van ander persone asof dit jou eie werk is.

*Plagiarism is the use of ideas, material and other intellectual property of another's work and to present is as my own.*

2. Ek erken dat die pleeg van plagiaat 'n strafbare oortreding is aangesien dit 'n vorm van diefstal is.

*I agree that plagiarism is a punishable offence because it constitutes theft.*

3. Ek verstaan ook dat direkte vertalings plagiaat is.


*I also understand that direct translations are plagiarism.*

4. Dienooreenkomstig is alle aanhalings en bydraes vanuit enige bron (ingesluit die internet) volledig verwys (erken). Ek erken dat die woordelike aanhaal van teks sonder aanhalingstekens (selfs al word die bron volledig erken) plagiaat is.

*Accordingly all quotations and contributions from any source whatsoever (including the internet) have been cited fully. I understand that the reproduction of text without quotation marks (even when the source is cited) is plagiarism*

5. Ek verklaar dat die werk in hierdie skryfstuk vervat, behalwe waar anders aangedui, my eie oorspronklike werk is en dat ek dit nie vantevore in die geheel of gedeeltelik ingehandig het vir bepunting in hierdie module/werkstuk of 'n ander module/werkstuk nie.

*I declare that the work contained in this assignment, except where otherwise stated, is my original work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.*

22546448	
Studentenommer / <i>Student number</i>	Handtekening / <i>Signature</i>
MC van der Berg	September 6, 2021
Voorletters en van / <i>Initials and surname</i>	Datum / <i>Date</i>

# Contents

<b>Declaration</b>	<b>i</b>
<b>List of Figures</b>	<b>iii</b>
<b>List of Tables</b>	<b>iv</b>
<b>Nomenclature</b>	<b>v</b>
<b>1. Low-side load control</b>	<b>1</b>
1.1. Literature . . . . .	1
1.2. Design . . . . .	1
1.3. Results . . . . .	1
<b>2. Bidirectional current measurement</b>	<b>2</b>
2.1. Introduction . . . . .	2
2.2. Design . . . . .	2
2.3. Results . . . . .	3
<b>Bibliography</b>	<b>6</b>
<b>A. GitHub Activity Heatmap</b>	<b>7</b>

# List of Figures

2.1. LTSPice output simulation graph . . . . .	4
2.2. LTSpice design schematic . . . . .	4
2.3. MY design and student number . . . . .	5

# List of Tables

# Nomenclature

## Variables and functions

$V_{BAT}$	Voltage battery source
$I_{LED}$	Current through LED
$V_{LED}$	Voltage over the LED
$V_{GS(th)}$	Gate Threshold Voltage
$V_{cc}$	Voltage source
$V_{out}$	Output voltage
$I_{LOAD}$	Current through the load
$R_{sense}$	Current sense resistor value
$V_{ref}$	Reference voltage
R	Resistor

## Acronyms and abbreviations

NPN Negative positive negative

MOSFET Metal–oxide–semiconductor field-effect transistor

LED Light emitting diode  $mV_{pk}$  millivolt peak

# Chapter 1

## Low-side load control

### 1.1. Literature

A load will be connected to the battery, this will allow the battery to discharge over the load. We want to be able to control this behaviour and thus need a switch. A low side switch will be build by only using a NPN MOSFET to control the discharge over the load.

### 1.2. Design

The load consists of 5 ultra bright LEDs connected in parallel with each other. The LEDs will be connected to the 7.2V source and the switch. The ultra bright LEDs datasheet [1] specifies a forward voltage drop of 3.2V. The maximum current that will flow through the load is 150mA, if 150mA flows through the load, each LED will receive a current of 30mA. This is the maximum rated forward current for the ultra bright LEDs according to the datasheet [1] this shouldn't damage the LEDs. The typical current of 100mA (20mA per LED) The NPN that will be used has a  $V_{GS(th)} = 2.1V$ . 5V will thus be sufficient to turn on the transistor [2].

Designing for one LED we thus use circuit analysis to do the following calculations:

$$V_{CC} = I_{LED} * R + V_{(LED)} \quad (1.1)$$

$$7.2 = (20m) * R + 3.2 \quad (1.2)$$

$$R = 200\Omega \quad (1.3)$$

I decided to use  $R = 220$  for safety and labs restrictions.

### 1.3. Results

The circuit worked as intended. The load could be controlled by the single NPN MOSFET, but because of resistor tolerance the voltage drop over the LEDs were not exact as the equation anticipated. For the following conditions:  $V_{CC} = 7.3V$ ;  $I = 100mA$ ;  $R = 220\Omega$ ; the led voltage was 2.91V. This is less than the typical forward voltage. This means that the LED would be as bright as they could be. But also means that the LED are more protected against higher currents.



# Chapter 2

## Bidirectional current measurement

### 2.1. Introduction

The RS -4Ah battery [3] has 4 different phases of charging, it should also be allowed to discharge over a load. The battery therefore has many modes it goes through and these modes need to be tracked to determine how the battery is behaving and how other components should behave according to the battery and users desires. A bidirectional current circuit is a circuit that measures the current flowing through a current sense resistor, a resistor so small that the voltage drop over it can be neglected, amplifies the voltage drop by using a amplifier and then sending out a output voltage that correlates to the current flowing through the sense resistor.

### 2.2. Design

The TLC213 [4] and current sensing resistor [5] was used to design a current sensing resistor. The TLC213 is selected because it has n build in gain of 50V. The TLC213 amplified the voltage difference over the current sensing current would output a voltage output  $V_{out}$  between 5V and 0V to determine if the battery is charging or discharging. The TLC213 has a gain of 50V/V and the following resistors where build into the component we received:  $R1=R2=1M\Omega$ ,  $R3=R4=20k\Omega$ . The reason these components have the same values are to minimize errors such as noise.

The current over the current sensing resistor( $1m\Omega$ ) will range from -150mA to 450mA and thus the center current (150mA) has to be at the center of the Voltage range. This will allow the best output swing. The following equations are used to determine the reference voltage( $V_{ref}$ ) to achieve the goal above:

$$V_{out} = I_{LOAD} * V_{diff} * gain + V_{ref} \quad (2.1)$$

Because we want the center current at the center voltage:

$$V_{out} = I_{LOAD} * R_{sense} + V_{ref} \quad (2.2)$$

$$2.5 = (0.1) * (0.15) * (50) + V_{ref} \quad (2.3)$$

$$V_{ref} = 1.75V \quad (2.4)$$

Because a  $V_{cc} = 5V$ , voltage division will be used to achieve the desired reference voltage. This means:

$$V_{ref} = V_{cc} * \frac{R6}{R6 + R5} \quad (2.5)$$

$$\frac{R6}{R6 + R5} = 0.35 \quad (2.6)$$

Choose  $R6 = 100k\Omega$ . This value is large enough to minimize current through the resistor and therefore minimizing power dissipation over the resistor as well.

$$R5 = \frac{R6}{0.35} - R6 \quad (2.7)$$

$$R5 = 185.7k\Omega \quad (2.8)$$

The output should be connected to a capacitor that will filter out the high frequency noise, however this capacitor should also be small enough as to not effect the transient response of the TLC213 too much. By running through many simulations in spice and seeing what is available in the labs, a capacitor of 4.7u has been chosen.

## 2.3. Results

The design requirement state the following:

1. The output voltage must be less than  $2mV_{pk}$ : The 4.7u capacitor is large enough to filter out high frequency noise the TLC213 might face. The maximum noise measured and seen on spice is 1,6mV which is less than  $2mV_{pk}$
2. The circuit response should respond to a change of 150mA in 2 seconds: The capacitor is small enough to achieve this requirement. The measured response is 1.79s, this is less than 2s.
3. Output voltage should be 3V for the given current range: The highest  $V_{out} = 4V$  and the lowest  $V_{out} = 1V$ , this means the output swing is 3V.
4. The voltage range must be 5V to 0V: This range was designed for as indicated above.  $V_{out}$  will never achieve 5V or 0V as the output swing does not allow it and this is also undesirable as this would hit the TLC213 Rail voltages.

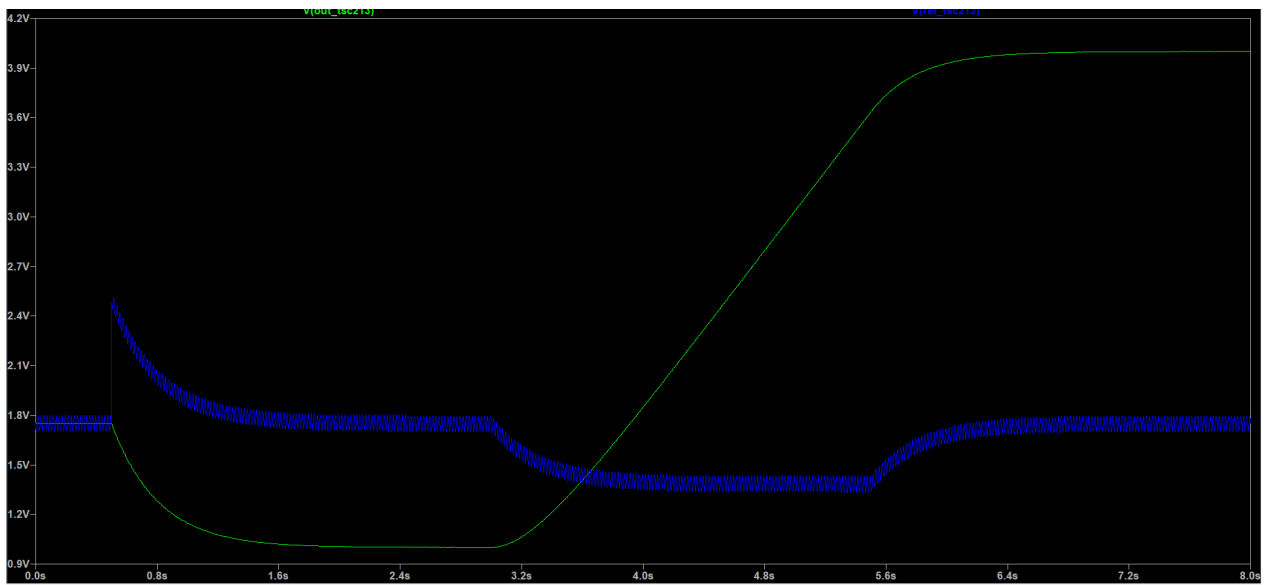


Figure 2.1: LTSpice output simulation graph


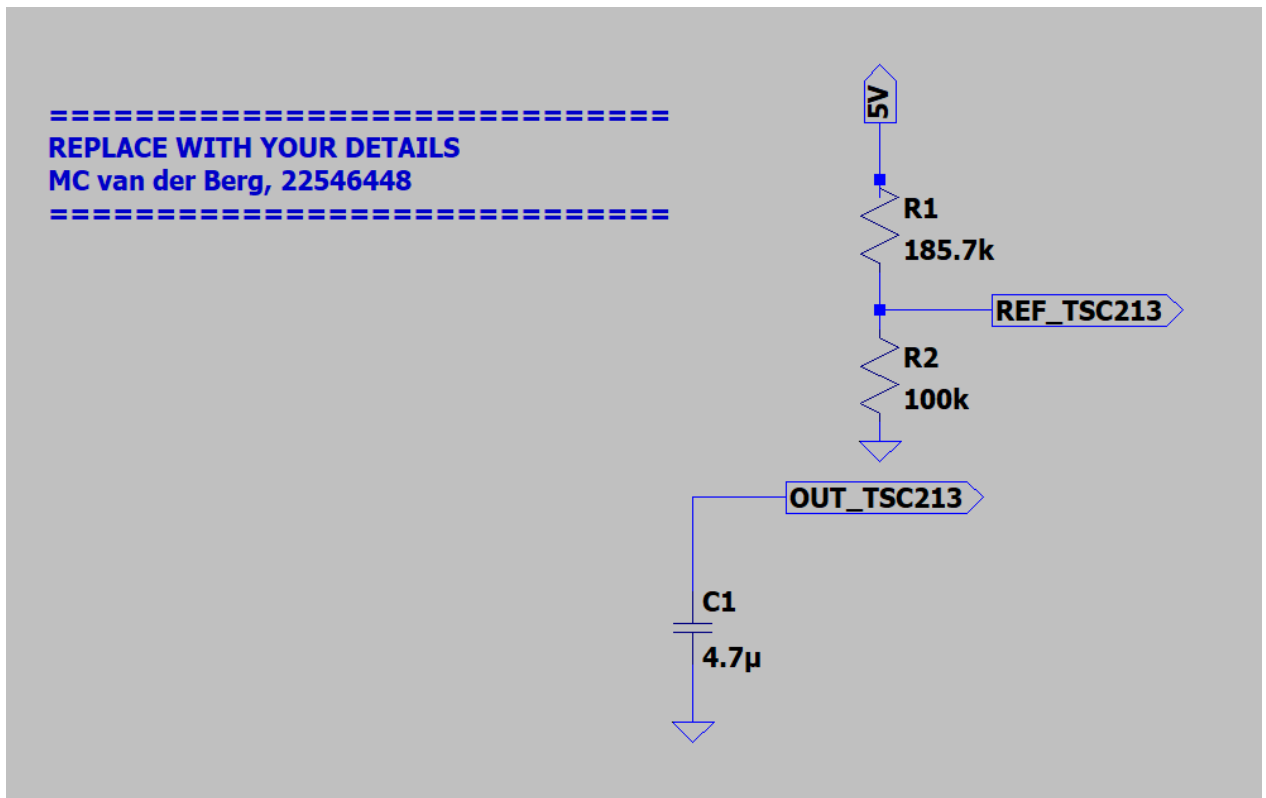


Figure 2.2: LTSpice design schematic

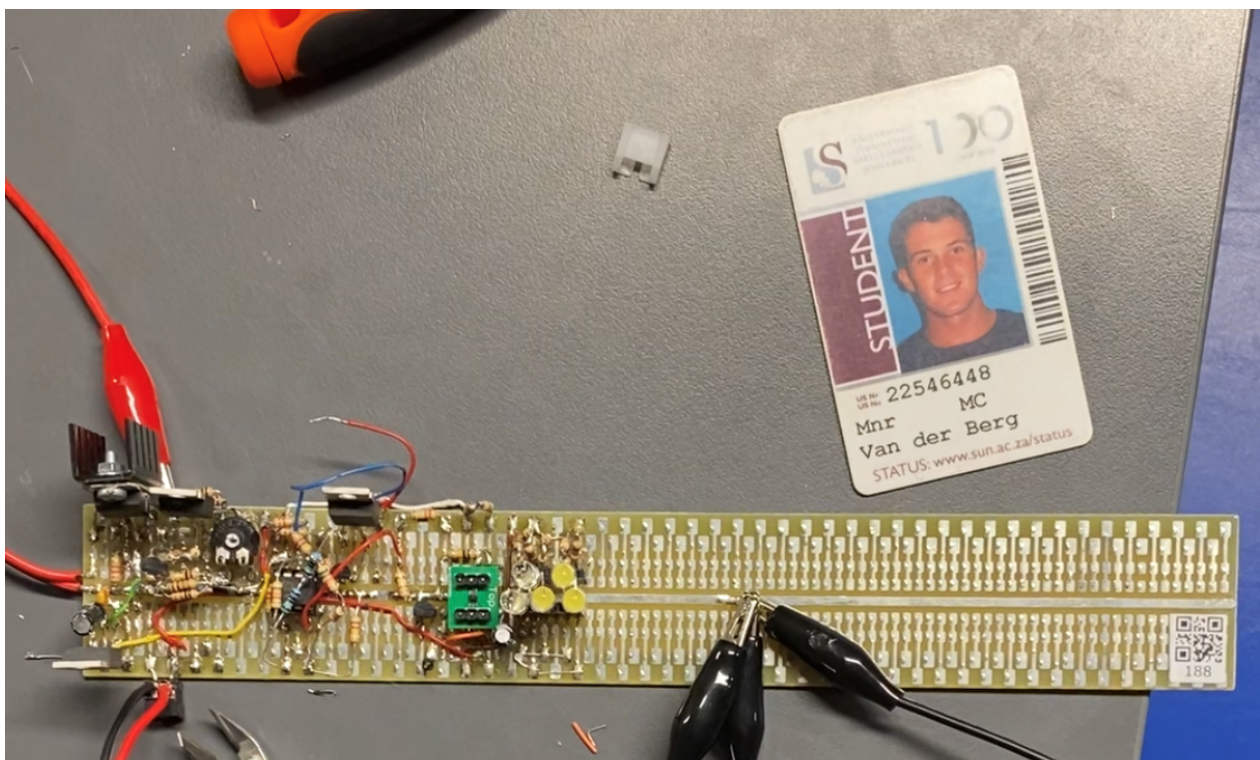

**Figure 2.3:** MY design and student number

# Bibliography

- [1] Cree, “Cree 5-mm round led,” 2021. [Online]. Available: [https://learn.sun.ac.za/pluginfile.php/2893565/mod\\_resource/content/0/Cree%205%20mm%20Round%20LED%20-%20Cool%20White.pdf](https://learn.sun.ac.za/pluginfile.php/2893565/mod_resource/content/0/Cree%205%20mm%20Round%20LED%20-%20Cool%20White.pdf)
- [2] O. semiconductors, “2n7000:2021,” 2021. [Online]. Available: [https://learn.sun.ac.za/pluginfile.php/2876543/mod\\_resource/content/0/2N7000.pdf](https://learn.sun.ac.za/pluginfile.php/2876543/mod_resource/content/0/2N7000.pdf)
- [3] R. Pro, “Battery:2021,” 2021. [Online]. Available: [https://learn.sun.ac.za/pluginfile.php/2876542/mod\\_resource/content/0/battery.pdf](https://learn.sun.ac.za/pluginfile.php/2876542/mod_resource/content/0/battery.pdf)
- [4] ST, “Tsc213:2021,” 2021. [Online]. Available: <https://www.overleaf.com/project/613388525b480fed594fe202>
- [5] RSPro, “Datasheet : Metal film resistor,” 2021. [Online]. Available: [https://learn.sun.ac.za/pluginfile.php/2893570/mod\\_resource/content/0/Current%20Sense%20Resistor.pdf](https://learn.sun.ac.za/pluginfile.php/2893570/mod_resource/content/0/Current%20Sense%20Resistor.pdf)

# Appendix A

## GitHub Activity Heatmap

*van der Berg Appendix*

